

# ELECTRICITY 2

---

---

# Contents

<b>I</b>	<b>Electric Current</b>	<b>1</b>
1	Current and Current Density	1
2	Continuity Law	1
<b>II</b>	<b>Ohm's and Joule's Law</b>	<b>2</b>
3	Electrical Mobility and Conductivity	2
4	Resistance	3
5	Electric Circuits	3
5.1	Power Sources/Generators	3
5.1.1	In Series	3
5.1.2	In Parallel	4
5.2	Loads	4
<b>III</b>	<b>Circuits Analysis Techniques</b>	<b>5</b>
6	Wye-Delta and Delta-Wye Transformations	5
7	Divider Circuits	6
7.1	Voltage Divider	6
7.2	Current Divider	7
8	Node Voltage Method	7

---

# Electric Current

## SECTION 1

### Current and Current Density

---

Electric charge in motion constitutes an electric current. In the steady flow of charge in a wire of cross-sectional area  $A$ , the total charge passing through this area in unit time is defined to be the electric current  $I$  at this place. If a total charge  $q$  flows through this area in time  $t$ , the current  $I$  is given by:

$$I = \frac{q}{t}. \quad (1.1)$$

where  $I$  is measured in Ampere. Sometimes it is also convenient to look at the density of the current we're observing over a certain area  $A$  called *current density*

$$J = \frac{I}{A}. \quad (1.2)$$

If the area in which the current is running through changes at points 1 and 2, the current between those 2 points remain constant ( $I_1 = I_2$ ) while the current density changes to become

$$\frac{J_1}{J_2} = \frac{A_2}{A_1}.$$

If a positively charged cloud of  $n$  particles moves through a space with speed  $v$  and charge  $q$ , we find that<sup>1</sup>

$$\vec{J} = nq\vec{v} = \rho_r\vec{v}. \quad (1.3)$$

The total current through a *slice* of space mentioned prior it calculated using

$$I = \iint_A \vec{J} \cdot d\vec{A}. \quad (1.4)$$

The volume element here is  $\vec{v} dA dt = d\tau$

<sup>1</sup>  $q$  can be positive or negative

## SECTION 2

### Continuity Law

---

The continuity law for current is

$$\nabla \cdot (\vec{J} + \vec{J}_c) = -\frac{\partial \rho_r}{\partial t}. \quad (2.1)$$

Where

$\vec{J}$  is the conduction current density.

$\vec{J}_c = \rho_\tau \vec{v}_\tau$  is the convection current density.

$\vec{v}_\tau$  is the velocity of the volume containing the particles.

There are 2 particular cases for the equation above

1. The volume is not moving ( $\vec{v}_\tau = 0 \implies \vec{J}_c = 0$ ). The continuity law of static structures is

$$\nabla \cdot \vec{J} = -\frac{\partial \rho_\tau}{\partial t}. \quad (2.2)$$

2. The volume is not moving and we are in a steady state, so the charge density of the particles doesn't change much as they are static so  $\partial \rho_\tau / \partial t = 0$  so

$$\oiint \vec{J} \cdot d\vec{A} = 0. \quad (2.3)$$

# Ohm's and Joule's Law

## PART II

### SECTION 3

## Electrical Mobility and Conductivity

The velocity of a charge carrier in an electric field  $\vec{E}$  is

$$\vec{v} = \mu \vec{E}. \quad (3.1)$$

where  $\mu$  is the mobility of the charge carrier.

The current density vector in a conductor with conductivity  $\sigma$  is said to be

$$\vec{J} = \sigma \vec{E}. \quad (3.2)$$

Ohm's law (doesn't really need an introduction)

$$U = RI. \quad (3.3)$$

where we can find  $R$  using

$$R = \frac{\rho l}{A}. \quad (3.4)$$

where  $A$  is the surface area of the resistor and  $l$  is the length of the conductor<sup>2</sup>.

$$^2 \sigma = \frac{1}{\rho}$$

### SECTION 4

## Resistance

---

The symbol of a resistive conductor is represented by



$$P = UI \quad (4.1)$$

$$W = Pt \quad (4.2)$$

Power loss due to Joule's law

$$P = I^2 R = \frac{U^2}{R} \quad (4.3)$$

$$W = I^2 R t \quad (4.4)$$

## SECTION 5

# Electric Circuits



---

## SUBSECTION 5.1
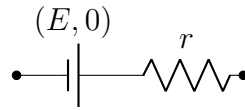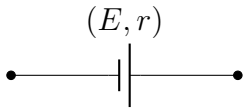
# Power Sources/Generators

---

A DC source is characterized by their electromotive force  $E$  and internal resistance  $r$





The voltage supplied by the source is

$$V_{\text{source}} = E - rI.$$

and it's efficiency is

$$\eta = 1 - \frac{rI}{E}.$$

### 5.1.1 In Series

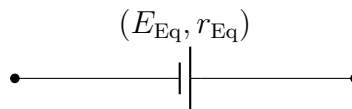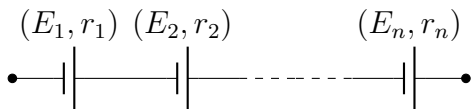


where

$$E_{\text{Eq}} = \sum_{i=1}^n E_i$$

$$r_{\text{Eq}} = \sum_{i=1}^n r_i$$

### 5.1.2 In Parallel

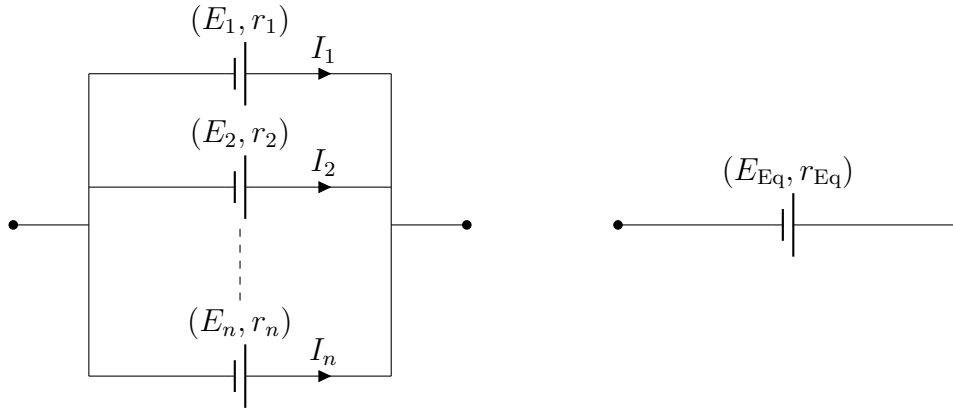

In case of *identical* sources:

$$I = \sum_{i=1}^n I_i$$

$$\frac{1}{r_{\text{Eq}}} = \sum_{i=1}^n \frac{1}{r_i}$$

and

$$V_{\text{source}} = E - r_{\text{Eq}} I.$$

## SUBSECTION 5.2

### Loads

An electrical load is an electrical component or portion of a circuit that consumes electric power. Electric loads are represented by a counter electromotive force  $e$  and internal resistance  $r'$  (with the exception of resistors)

All formulas for generators are the same as loads with the exception of the efficiency

$$\eta = 1 - \frac{r' I}{U}.$$

# Circuits Analysis Techniques

## PART III

Terminology:

**Node** A point where two or more circuit elements join.

**Essential node** A node where three or more circuit elements join.


**Branch** A path that connects two nodes

**Loop** A path whose last node is the same as the starting node

**Mesh** A loop that does not enclose any other loops

- **KVL:** the algebraic sum of all the voltages around any closed path in a circuit equals zero.
- **KCL:** the algebraic sum of all the currents at any node in a circuit equals zero.

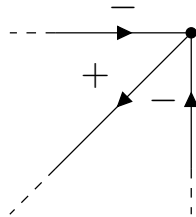
To use Kirchhoff's current law, an algebraic sign corresponding to a reference direction must be assigned to every current at the node. Assigning a positive sign to a current leaving a node requires assigning a negative sign to a current entering a node.




## SECTION 6
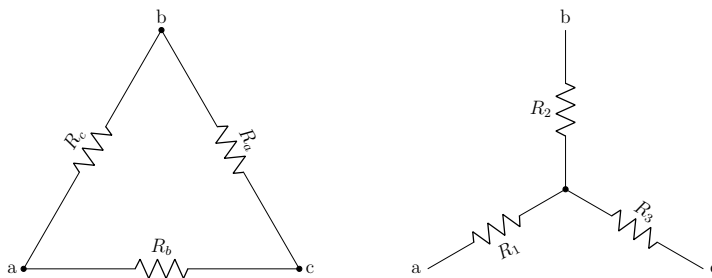
### Wye-Delta and Delta-Wye Transformations

This transformation of a set of resistors configured in the shape of the letter  $\Delta$  to a configuration of a shape of the letter Y.



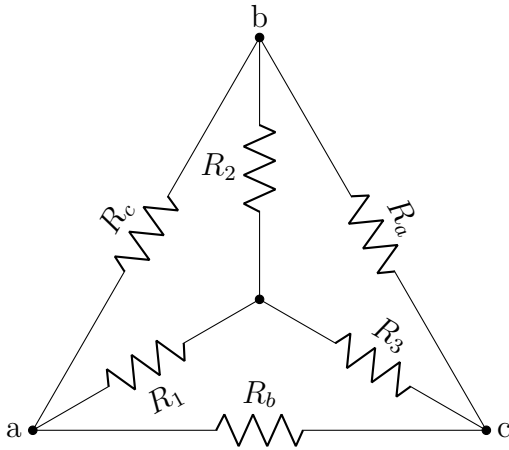To find the equivalent resistances we apply



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


## SECTION 7

# Divider Circuits

## SUBSECTION 7.1

# Voltage Divider

At times especially in electronic circuits developing more than one voltage level from a single voltage supply is necessary. One way of doing this is by using a voltage-divider circuit.

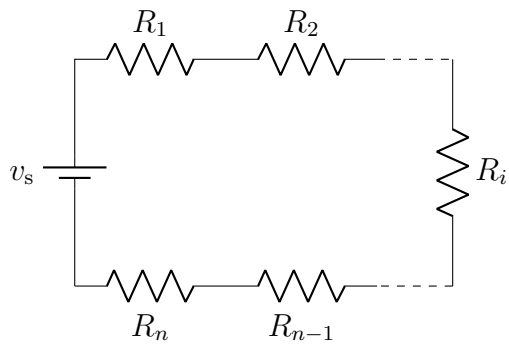


**Figure 3.** An  $n$  resistor voltage divider

$$v_i = v_s \frac{R_i}{\sum_{j=1}^n R_j}.$$



## Current Divider

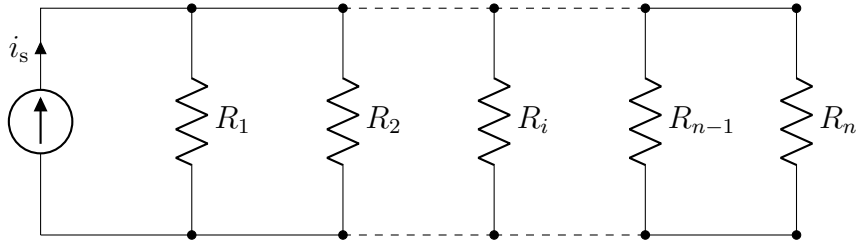


**Figure 3.** An  $n$  resistor current divider

$$i_i = i_s \frac{R_{\text{Eq}}}{R_i}.$$
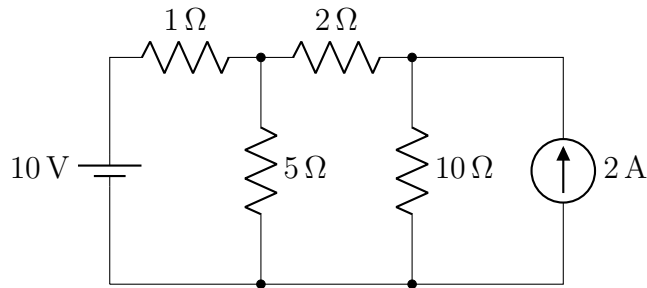
## Node Voltage Method


We introduce the node-voltage method by using the essential nodes of the circuit.

To better understand node voltage method, we will apply directly on a circuit. Consider the following circuit:




To find the voltages across the resistors are

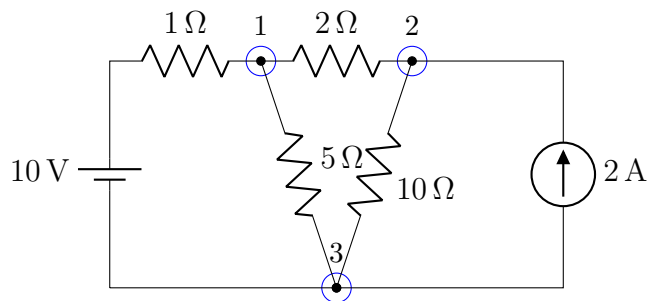1. Assign the essential nodes (nodes with 3 or more branches):




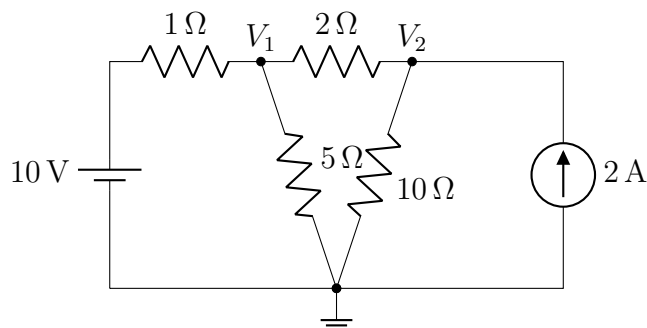- Choose a reference node: select one of the essential nodes to be a reference. Usually we choose the lowest node. The assign voltages to the other nodes.




- Apply KCL at each node to determine the voltage. For example let's look at node 1:

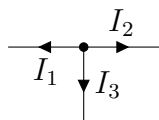Assume that there are currents leaving the node from all directions and that carry the voltage  $V_1$  with them where by KCL



$$I_1 + I_2 + I_3 = 0.$$

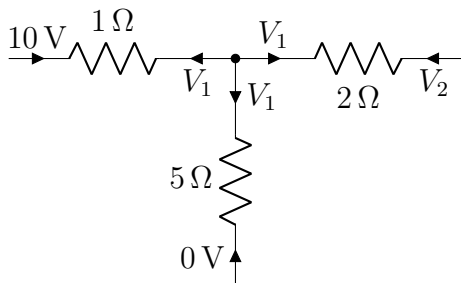We let these currents carry our voltage  $V_1$  with them, now we find the values of the currents. So the equation for node 1 is



$$\frac{V_1 - 10}{1} + \frac{V_2 - V_1}{2} + \frac{V_1 - 0}{5} = 0.$$

Similarly for node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2 - 0}{10} - 2 = 0.$$

By simply solving the equations we get

$$\begin{aligned} V_1 &= 9.09 \text{ V} \\ V_2 &= 10.91 \text{ V} \end{aligned}$$