

Magnetism

Semester 5

Ahmad Abu Zainab

Contents


Chapter 1	Electromagnetic Waves _____	Page 2 _____
	Poynting Vector — 2 • Maxwell's Equations — 3	
Chapter 2	Optics _____	Page 4 _____
	Reflection — 4 • Refraction — 4	
2.1	Young's Double Slit Experiment	5
2.2	Diffraction Grating	6
Chapter 3	Transmission Lines _____	Page 7 _____
3.1	The Phasor	7
3.2	The Role of Wavelength	7
3.3	TL lumped element model	7
3.4	The Telegrapher's Equations	8
3.5	Lossless Transmission Line	9
3.6	Voltage Reflection Coefficient	9
3.7	Special Line Conditions	10
3.8	Standing Waves	10

Chapter 1

Electromagnetic Waves

Electromagnetic waves are waves that are created by oscillating electric and magnetic fields. The electric and magnetic fields are perpendicular to each other and to the direction of propagation of the wave. They travel at a speed of $c = 299792458$ m/s in a vacuum. The frequency of the wave is given by $f = \frac{c}{\lambda}$ where λ is the wavelength of the wave.

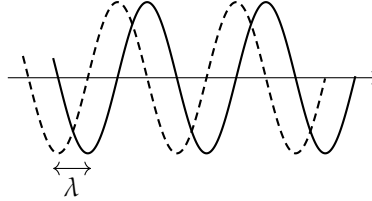The wavelength is the distance between two consecutive peaks of the wave.



The wave moves a distance x in a time t with a speed

$$v = \frac{x}{t} = \frac{\omega}{k} = \frac{\lambda}{T} = \lambda f.$$

$$\lambda = \frac{2\pi}{f}.$$

The equation of the wave is given by

$$y = A \sin(\omega t - kx + \phi).$$

The intensity of the wave is given by

$$I = \frac{P}{4\pi r^2}.$$

1.0.1 Poynting Vector

The Poynting vector is a vector that represents the energy flux of the wave. It is given by

$$\vec{S} = \frac{1}{\mu_0} \vec{E} \times \vec{B}.$$

However, since \vec{B} are perpendicular to \vec{E} then

$$S = \frac{1}{\mu_0} EB.$$

and since

$$c = \frac{E}{B}.$$

then

$$S = \frac{c}{\mu_0} B^2 = \frac{1}{c\mu_0} E^2.$$

1.0.2 Maxwell's Equations

$$\begin{aligned}\frac{\partial \vec{\mathbf{E}}}{\partial x} &= -\frac{\partial \vec{\mathbf{B}}}{\partial t} \\ \frac{\partial \vec{\mathbf{B}}}{\partial x} &= -\varepsilon_0 \mu_0 \frac{\partial \vec{\mathbf{E}}}{\partial t}\end{aligned}$$

Chapter 2

Optics

The equation of an EM wave is given by

$$\vec{\mathbf{E}} = E_0 \sin(\omega t - kx) \hat{j}.$$

Noting that electric field typically have all directions, whenever an non-polarised electric field hits a polariser, only the electric field components that are along the line of polarization are allowed to pass while all others are absorbed. If the electric field direction is perpendicular to the line of polarization then it is entirely absorbed while the electric field vectors that have an angle $\theta < \pi/2$ then only the projection of that vector on the polarization line will not be absorbed.


Given a polariser with angle α then the electric field $\vec{\mathbf{E}}$ hitting that polariser has an equation

$$\vec{\mathbf{E}} = \underbrace{E \sin \alpha \hat{\mathbf{u}}_1}_{\text{transmitted}} + \underbrace{E \cos \alpha \hat{\mathbf{u}}_2}_{\text{absorbed}}.$$

2.0.1 Reflection

The angle of incidence is equal to the angle of reflection.


$$\theta_i = \theta_r.$$

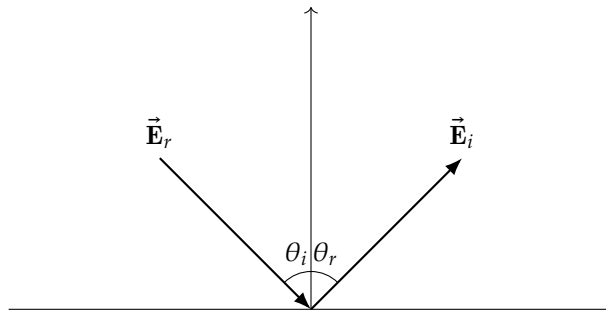

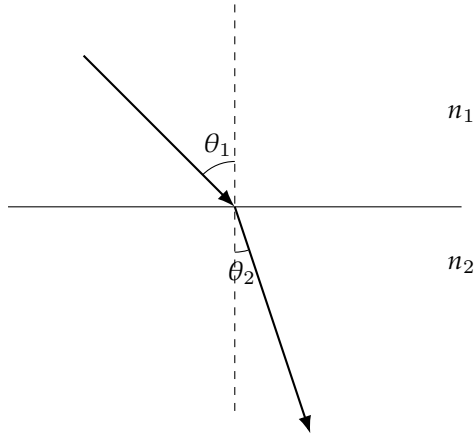2.0.2 Refraction

Snell's law

$$n_1 \sin \theta_1 = n_2 \sin \theta_2.$$




This implies that if $n_1 < n_2$ then $\theta_1 > \theta_2$.

Definition 2.0.1: Critical Angle

The critical angle is the maximum angle of refraction where the refracted ray goes back in the incident medium.
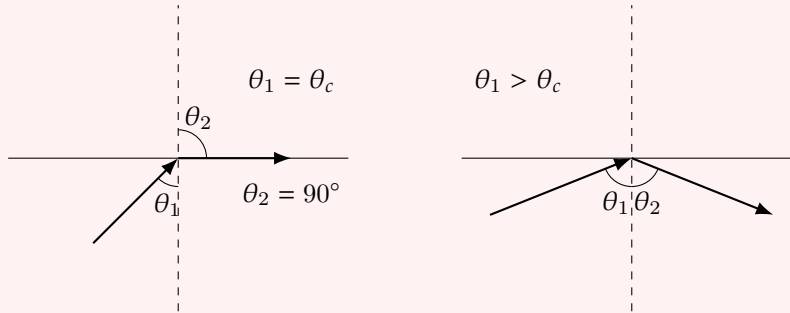
$$\theta_c = \sin^{-1} \left(\frac{n_2}{n_1} \right).$$



$$v = \frac{c}{n}.$$

$$\text{Speed of light in a medium} = \frac{1}{\sqrt{\mu\epsilon}}$$

$$\text{Speed of light in a vacuum} = \frac{1}{\sqrt{\mu_0\epsilon_0}}$$

$$\text{Refractive index} = \sqrt{\mu_r\epsilon_r}$$

$$\frac{n_1}{n_2} = \frac{v_2}{v_1}.$$

2.1 Young's Double Slit Experiment

$$d \sin \theta = m\lambda.$$

$$\Delta x = \frac{m\lambda L}{d}.$$

Bright fringes are where the path difference is an integer multiple of the wavelength.

$$x = \frac{m\lambda L}{d}.$$

Dark fringes are where the path difference is an odd multiple of half the wavelength.

$$x = \frac{(2m + 1)\lambda L}{2d}.$$

Where m is an integer, d is the distance between the slits, λ is the wavelength of the light, L is the distance between the slits and the screen, and x is the distance between the central bright fringe and the m th bright fringe.

2.2 Diffraction Grating

$$\sin \theta_1 = \frac{\lambda}{a}.$$

$$\sin \theta_n = n \frac{\lambda}{d}.$$

Chapter 3

Transmission Lines

3.1 The Phasor

The phasor is a complex number that represents the amplitude and phase of a sinusoidal function. It is given by 2 forms

$$\text{Rectangular form} = A \cos(\omega t + \varphi) + jA \sin(\omega t + \varphi).$$

$$\text{Polar form} = Ae^{j(\omega t + \varphi)} = A/\underline{\omega t + \varphi}.$$

3.2 The Role of Wavelength

In a transmission line, the wavelength of the signal can affect the impedance of the line. The voltage at the source ($V_{AA'}$) is given by

$$V_{AA'} = V_0 \cos \omega t.$$

The voltage at the load ($V_{BB'}$) (assuming no losses across the transmission line) is given by


$$V_{BB'} = V_0 \cos(\omega t - \varphi_0).$$

$$\varphi_0 = \frac{\omega l}{c}.$$

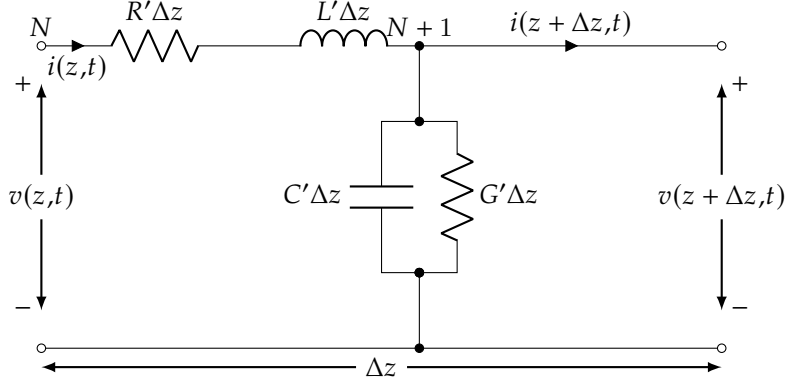3.3 TL lumped element model

We can model a transmission line using a series of resistors, inductors, and capacitors. The model is given by 4 parameters

$$\begin{aligned} R' &= \text{Resistance per unit length } [\Omega/\text{m}] \\ L' &= \text{Inductance per unit length } [\text{H}/\text{m}] \\ C' &= \text{Capacitance per unit length } [\text{F}/\text{m}] \\ G' &= \text{Conductance per unit length } [\text{S}/\text{m}] \end{aligned}$$



Parameter	Coaxial	Two-Wire	Parallel-Plate	Unit
R'	$\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_s}{\pi d}$	$\frac{2R_s}{w}$	Ω/m
L'	$\frac{\mu}{2\pi} \ln b/a$	$\frac{\mu}{\pi} \ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$	H/m
G'	$\frac{2\pi\sigma}{\ln b/a}$	$\frac{\pi\sigma}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$	S/m
C'	$\frac{2\pi\epsilon}{\ln b/a}$	$\frac{\pi\epsilon}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$	F/m

Where μ , ϵ , and σ are the permeability, permittivity, and conductivity of the medium respectively. $R_s = \sqrt{\pi f \mu_c / \sigma_c}$ is the resistance of the conductor, a is the radius of the inner conductor, b is the radius of the outer conductor, D is the distance between the two wires, d is the diameter of the wire, w is the width of the plate, and h is the height of the plate.

3.4 The Telegrapher's Equations

The wave equation is given by

$$\frac{d^2 \tilde{V}(z)}{dz^2} - (R' + j\omega L')(G' + j\omega C') \tilde{V}(z) = 0.$$

Thus, we define the complex propagation constant γ as

$$\gamma = \alpha + j\beta.$$

Where α is the attenuation constant and β is the phase constant.

$$\begin{aligned} \alpha &= \text{Re}(\gamma) \quad [\text{Np}/\text{m}] \\ \beta &= \text{Im}(\gamma) \quad [\text{rad}/\text{m}] \end{aligned}$$

In uncoupled form, the telegrapher's equations are given by

$$\begin{aligned} \frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) &= 0 \\ \frac{d^2 \tilde{I}(z)}{dz^2} - \gamma^2 \tilde{I}(z) &= 0 \end{aligned}$$

The general solution to the wave equation is given by

$$\begin{aligned}\tilde{V}(z) &= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ \tilde{I}(z) &= I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}\end{aligned}$$

Where V_0^+ and I_0^+ are the incident voltage and current respectively and V_0^- and I_0^- are the reflected voltage and current respectively.

The characteristic impedance of the transmission line is given by

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad [\Omega].$$

3.5 Lossless Transmission Line

In a lossless transmission line, the resistance and conductance per unit length are zero. I.E. $R' \ll \omega L'$ and $G' \ll \omega C'$. Thus, the characteristic impedance is given by

$$\begin{aligned}\alpha &= 0 \\ \beta &= \omega \sqrt{L'C'} = \omega \sqrt{\mu \epsilon} \\ Z_0 &= \sqrt{\frac{L'}{C'}} \\ \lambda &= \frac{2\pi}{\beta} = \frac{2\pi}{\omega \sqrt{L'C'}} \\ u_p &= \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\mu \epsilon}} \quad [\text{m/s}]\end{aligned}$$

3.6 Voltage Reflection Coefficient

The voltage reflection coefficient is given by

$$\begin{aligned}\Gamma &= \frac{V_0^-}{V_0^+} \\ &= \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{z_L - 1}{z_L + 1}\end{aligned}$$

Where $z_L = Z_L/Z_0$ is the load impedance in terms of the characteristic impedance.

We represent the voltage and current on the transmission line as

$$V_0^- = \Gamma V_0^+.$$

$$\begin{aligned}\tilde{V}(z) &= V_0^+ \left(e^{-j\beta z} + \Gamma e^{j\beta z} \right) \\ \tilde{I}(z) &= \frac{V_0^+}{Z_0} \left(e^{-j\beta z} - \Gamma e^{j\beta z} \right)\end{aligned}$$

And their magnitudes are given by

$$|\tilde{V}(d)| = |V_0^+| \left[1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}$$

$$|\tilde{I}(d)| = \frac{|V_0^+|}{Z_0} \left[1 + |\Gamma|^2 - 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}$$

where $d = -z$


3.7 Special Line Conditions

1. Matched Line: $Z_L = Z_0 \Rightarrow \Gamma = 0$ $V_{\text{ref}} = 0$
2. Open Circuit: $Z_L = \infty \Rightarrow \Gamma = 1$ $V_{\text{ref}} = V_{\text{inc}}$
3. Short Circuit: $Z_L = 0 \Rightarrow \Gamma = -1$ $V_{\text{ref}} = -V_{\text{inc}}$


Load	$ \Gamma $	θ_r
$Z_L = (r + jx)Z_0$	$\left[\frac{(r-1)^2 + x^2}{(r+1)^2 + x^2} \right]^{1/2}$	$\tan^{-1} \left(\frac{x}{r-1} \right) - \tan^{-1} \left(\frac{x}{r+1} \right)$
$Z_L = Z_0$	0	Irrelevant
(short)	1	$\pm\pi$ (phase opposite)
(open)	1	0
$jX = j\omega L$	1	$\pm\pi - 2 \tan^{-1} x$
$jX = -\frac{j}{\omega C}$	1	$\pm 2 \tan^{-1} x$

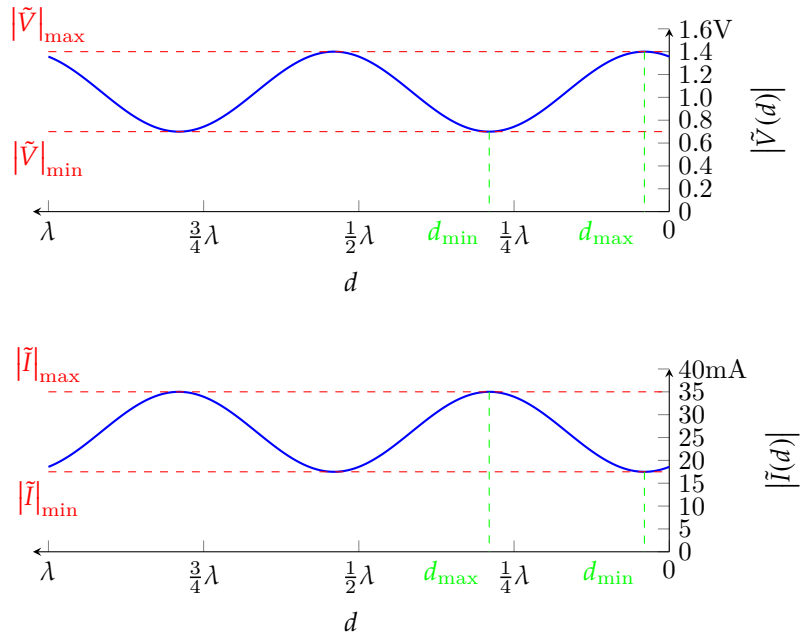3.8 Standing Waves

Standing waves are waves that do not propagate. They are formed when two waves of the same frequency and amplitude travel in opposite directions.



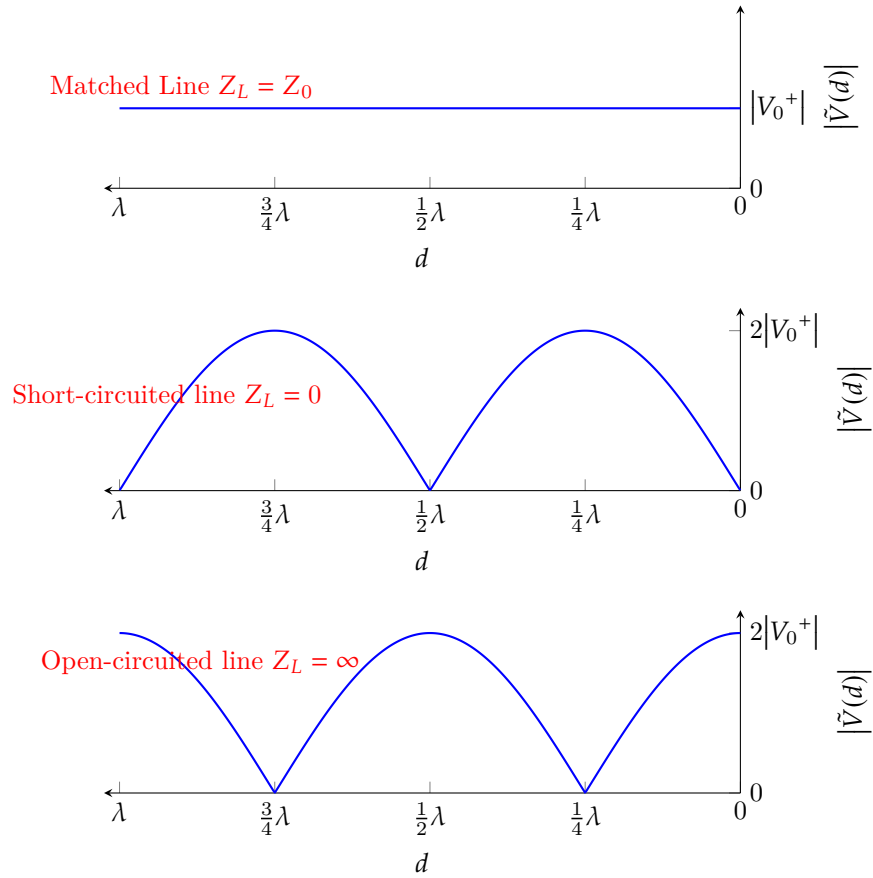The figure above, shows the voltage and current on a transmission line. The voltage and current are in phase opposition. This general graph applies for all values of Γ with the exception of 3 lines conditions.



We want to find the minimum and maximum values of the voltage magnitude.

$$d_{\max} = \frac{\theta_r + 2n\pi}{2\beta} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}$$

$$\begin{cases} n = 1, 2, 3, \dots & \text{if } \theta_r < 0 \\ n = 0, 1, 2, \dots & \text{if } \theta_r \geq 0 \end{cases}$$

$$d_{\min} = \begin{cases} d_{\max} + \frac{\lambda}{4} & \text{if } d_{\max} < \lambda/4 \\ d_{\max} - \frac{\lambda}{4} & \text{if } d_{\max} \geq \lambda/4 \end{cases}$$

The ratio of $|\tilde{V}|_{\max}$ to $|\tilde{V}|_{\min}$ is called the voltage standing wave ratio S (VSWR or SWR) and is given by

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}.$$

And it represents the mismatch between the load and the transmission line. For a matched load line $\Gamma = 0$ and $S = 1$. For an open circuit or short circuit line $\Gamma = 1$ and $S = \infty$.

Note:-

The average power on a transmission line is given by

$$P_{\text{avg}} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma|^2).$$